



**NATIONAL INSTITUTE OF BUSINESS MANAGEMENT**

**DIPLOMA IN SOFTWARE ENGINEERING 17.2F**

**COMPUTER TECHNOLOGY DSE-2-4-05**

21<sup>st</sup> May 2018

9.00 am – 12.00 noon

Answer *all* questions.

*Electronic calculators are allowed.*

Time: THREE hours.

**PART A-DIGITAL ELECTRONICS**

**Question 1**

- i. Simplify the following expressions using De Morgan's Law.

a.  $Z = \overline{\bar{A} \cdot \bar{B}} + \overline{\bar{A} \cdot \bar{B} \cdot C}$

b.  $Z = \overline{A + \bar{B} \cdot \bar{C} + C \cdot D + \bar{B} \cdot \bar{C}}$

c.  $Z = \overline{(A \cdot B + \bar{B} \cdot \bar{C}) \cdot (\bar{A} \cdot \bar{B} + \bar{A} \cdot B \cdot \bar{C} + ABC)}$

(06 Marks)

- ii.  $Z = f(A, B, C, D)$

$Z=1$  for the minterms (0, 2, 5, 7, 8, 13)

$Z=$  don't care for the minterms (10, 15)

$Z = 0$  for the remaining minterms.

Simplify  $Z$  using:

i) K- map method

(02 Marks)

ii) Tabular method

(04 Marks)

- iii. Explain the importance of Boolean expression simplification in Digital Circuit Designing.

(02 Marks)

## Question 2

- i. Draw the truth table of Full Adder and implement the circuit using basic logic gates.

(04 Marks)

- ii. An assembly line has 3 failsafe sensors and 1 emergency shutdown switch. The assembly line will be deactivated by switching off the emergency shutdown switch if anyone of the following conditions occur.

- If the emergency switch is pressed, the system shuts down.
- If sensor 1 and sensor 2 are activated at the same time, the system shuts down
- If sensor 2 and sensor 3 are activated at the same time, the system shuts down.
- If all three sensors are activated at the same time, the system shuts down.

- a. Determine the truth table for the circuit.

(02 Marks)

- b. Obtain the simplified

- i. SOP expression

(02 Marks)

- ii. POS expression

(02 Marks)

- c. Implement the circuit using

- i. **NAND** gates only.

(03 Marks)

- ii. 4:1 Multiplexer.


(03 Marks)

- iii. Explain the operation of 1:4 De multiplexer using a diagram.

(04 Marks)

### Question 3

 - i. Draw the output waveform Q of a positive edge triggered SR flip flop. Assume that the initial value of the flip flop is 0. (02 Marks)



- ii. Complete the truth table of J-K flip flop and derive its excitation table. (04 Marks)
- iii. Design a 3-bit counter to count the bit sequence 0,2,4,6. Use positive edge triggered J-K flip flops. (06 Marks)
- iv. Three edge-triggered JK flip flops in a synchronous circuit have the following input conditions:

$$J_A = Q_C$$

$$K_A = 1$$

$$J_B = 1$$

$$K_B = \bar{Q}_A \cdot Q_C$$

$$J_C = Q_B$$

$$K_C = 1$$

Assume that the initial state is  $Q_A = 0$   $Q_B = 1$   $Q_C = 1$ . Find the count sequence. (04 Marks)

## PART B- PHYSICAL ELECTRONICS

### Question 4


- Briefly explain how N-Type semi-conductors are formed using its crystal structure. (03 Marks)
- Explain the reversed biased mode of the P-N junction. (03 Marks)
- Draw the Volt-Ampere characteristics of a practical diode and mark  $I_s$  (Reverse Saturation Current), PIV (Peak Inverse Voltage) and  $V_b$  (Forward Biased Voltage) on the curve. (02 Marks)
- Draw the circuit diagram of Half Wave Rectifier and explain the operation of it. (04 Marks)

### Question 5


- Draw the graph of input characteristics of a transistor. (03 Marks)
- Consider the following circuit and obtain the operating mode of the transistor. Hence calculate  $I_B$ ,  $I_C$  and  $V_{CE}$ . Assume that the transistor is made out of Silicon. (12 Marks)

Material	$V_{CE}(\text{sat})$	$V_{BE}(\text{sat})$	$V_{BE}(\text{act})$	$V_{BE}(\text{cut in})$
Si	0.2V	0.8V	0.7V	0.5V
Ge	0.1V	0.3V	0.2V	0.1V

$\beta$	$R_B$	$R_C$	$V_{CC}$	$V_{BB}$
100	200k $\Omega$	2k $\Omega$	10V	5V

 

 6. Consider the circuit in figure 2 and the characteristic curve of the JFET in figure 3 .If  $V_{DD} = 12V$ ,  $V_{GG} = 1.2V$ ,  $R_G = 2k\Omega$ ,  $R_D = 2k\Omega$ .



- What is the type of the given JFET? (01 Mark)
- Indicate the three regions of the characteristic curve. (01 Mark)
- Calculate Gate-Source voltage. (03 Marks)
- Obtain an equation for the load line of the circuit and plot it over the given characteristic curve. (03 Marks)
- Hence identify the operating mode of the JFET and find the coordinate of the operating point. (02 Marks)

There are many digital logic families.

- Explain two important characteristics of Digital Logic Families briefly. (02 Marks)
- Consider the following digital logic circuit. Then identify its logic family and show that it is an AND gate by using a suitable truth table. (03 Marks)

